

```
% ECSE 563 assignmenet 1
% Ali Seifeldin
% https://github.com/Bakalala/MGCILL-ECSE-563
```

% Question 1

```
% Load parameters for IEEE9_A1
run('ieee9_A1.m');
```

```
Y = admittance(nfrom, nto, r, x, b)
```

```
Y = 9x9 complex
0.0000 -17.3611i    0.0000 + 0.0000i    0.0000 + 0.0000i    0.0000 +17.3611i ...
0.0000 + 0.0000i    0.0000 -16.0000i    0.0000 + 0.0000i    0.0000 + 0.0000i
0.0000 + 0.0000i    0.0000 + 0.0000i    0.0000 -17.0648i    0.0000 + 0.0000i
0.0000 +17.3611i    0.0000 + 0.0000i    0.0000 + 0.0000i    3.3074 -39.3089i
0.0000 + 0.0000i    0.0000 + 0.0000i    0.0000 + 0.0000i    -1.9422 +10.5107i
0.0000 + 0.0000i    0.0000 + 0.0000i    0.0000 +17.0648i    0.0000 + 0.0000i
0.0000 + 0.0000i    0.0000 + 0.0000i    0.0000 + 0.0000i    0.0000 + 0.0000i
0.0000 + 0.0000i    0.0000 +16.0000i    0.0000 + 0.0000i    0.0000 + 0.0000i
0.0000 + 0.0000i    0.0000 + 0.0000i    0.0000 + 0.0000i    -1.3652 +11.6041i
```

% Calculate V and convert to polar

```
V = Y \ Iint;
Vpolar_original = [abs(V), rad2deg(angle(V))]
```

```
Vpolar_original = 9x2
1.0001    -0.0060
1.0001     9.6638
1.0001     4.7653
0.9871    -2.4100
0.9756    -4.0208
1.0035     1.9178
0.9858     0.6152
0.9963     3.7918
0.9578    -4.3537
```

% Question 2

```
% Load parameters for IEEE9_A1
run('ieee9_A1.m');
```

% Impedance matrix

```
Z = impedance(nfrom, nto, r, x, b)
```

```
Z = 9x9 complex
0.0103 - 0.6225i    -0.0046 - 0.7614i    -0.0061 - 0.7644i    0.0103 - 0.6801i ...
-0.0046 - 0.7614i    0.0089 - 0.6194i    0.0001 - 0.7484i    -0.0046 - 0.7614i
-0.0061 - 0.7644i    0.0001 - 0.7484i    0.0096 - 0.6249i    -0.0061 - 0.7644i
0.0103 - 0.6801i    -0.0046 - 0.7614i    -0.0061 - 0.7644i    0.0103 - 0.6801i
0.0032 - 0.7208i    -0.0056 - 0.7686i    -0.0037 - 0.7475i    0.0032 - 0.7208i
-0.0061 - 0.7644i    0.0001 - 0.7484i    0.0096 - 0.6835i    -0.0061 - 0.7644i
-0.0060 - 0.7684i    0.0047 - 0.7150i    0.0035 - 0.7268i    -0.0060 - 0.7684i
-0.0046 - 0.7614i    0.0089 - 0.6819i    0.0001 - 0.7484i    -0.0046 - 0.7614i
0.0053 - 0.7178i    -0.0029 - 0.7439i    -0.0058 - 0.7691i    0.0053 - 0.7178i
```

```

% Question 3
% Load parameters for IEEE9_A1

run('ieee9_A1.m');

Zf = 0;
for idfault = 1:size(Y,1)
    idfault
    [If, Vf] = fault(Y, Iint, idfault, Zf);
    Ifpolar = [abs(If), rad2deg(angle(If))]
    Vpolar = [abs(Vf), rad2deg(angle(Vf))]
    Vpolar_diff = Vpolar_original - Vpolar
    RMSE = rmse(Vpolar_original, Vpolar_diff, 1)

end

```

```

idfault =
1
Ifpolar = 1x2
    1.6064    89.0450
Vpolar = 9x2
    0.0000   -90.0000
    0.3072   140.4306
    0.2573   153.8770
    0.1136  -159.4655
    0.1924  -163.6047
    0.2336   164.1530
    0.2516   170.6862
    0.2471   157.7116
    0.2076  -162.6161
Vpolar_diff = 9x2
    1.0001    89.9940
    0.6929  -130.7668
    0.7428  -149.1117
    0.8735   157.0555
    0.7832   159.5839
    0.7699  -162.2352
    0.7342  -170.0710
    0.7492  -153.9198
    0.7502   158.2624
RMSE = 1x2
    0.2192   153.1490
idfault =
2
Ifpolar = 1x2
    1.6146    98.8370
Vpolar = 9x2
    0.2819  -139.9119
    0.0000  -14.0362
    0.2225  -152.4966
    0.3200  -135.8400
    0.3568  -135.4784
    0.2443  -141.4490
    0.2324  -131.4385
    0.1489  -127.9122
    0.3433  -132.6227
Vpolar_diff = 9x2
    0.7182   139.9059
    1.0001    23.7000

```

```

0.7776 157.2619
0.6671 133.4300
0.6188 131.4576
0.7592 143.3667
0.7534 132.0537
0.8474 131.7040
0.6145 128.2690
RMSE = 1x2
0.2609 129.5585
idfault =
3
Ifpolar = 1x2
1.6003 93.8833
Vpolar = 9x2
0.2328 -161.6563
0.2262 157.4961
0.0000 -172.8750
0.2614 -153.9779
0.2632 -146.9710
0.1036 -147.3795
0.1893 -157.0800
0.2014 -175.6068
0.3105 -151.7848
Vpolar_diff = 9x2
0.7673 161.6503
0.7739 -147.8324
1.0001 177.6403
0.7257 151.5680
0.7124 142.9502
0.8999 149.2973
0.7965 157.6952
0.7950 179.3985
0.6473 147.4311
RMSE = 1x2
0.2177 158.6066
idfault =
4
Ifpolar = 1x2
1.4513 86.7213
Vpolar = 9x2
0.0437 71.4432
0.2649 116.1588
0.1906 125.4079
0 0
0.0726 -169.4621
0.1484 134.5347
0.1518 146.8558
0.1739 128.6497
0.0880 -166.3063
Vpolar_diff = 9x2
0.9565 -71.4492
0.7352 -106.4950
0.8095 -120.6426
0.9871 -2.4100
0.9030 165.4413
0.8551 -132.6169
0.8340 -146.2406
0.8224 -124.8579
0.8698 161.9526
RMSE = 1x2
0.1478 127.7655
idfault =
5
Ifpolar = 1x2

```

```

1.4325    85.0458
Vpolar = 9x2
0.0893    108.9139
0.2925    112.1503
0.1938    111.0682
0.0607    134.8647
0.0000    180.0000
0.1459    115.7534
0.1552    133.1643
0.1974    121.1475
0.1133    169.6861
Vpolar_diff = 9x2
0.9109   -108.9199
0.7076   -102.4865
0.8062   -106.3029
0.9264   -137.2747
0.9756   -184.0208
0.8576   -113.8356
0.8306   -132.5491
0.7990   -117.3557
0.8445   -174.0398
RMSE = 1x2
0.1605    134.1501
idfault =
6
Ifpolar = 1x2
1.4681    91.1114
Vpolar = 9x2
0.1227   -173.9318
0.1847    127.5631
0.0499     97.2527
0.1464   -158.1995
0.1500   -145.8366
0         0
0.0824   -169.3758
0.1134    156.9618
0.1942   -153.6850
Vpolar_diff = 9x2
0.8774    173.9258
0.8154   -117.8993
0.9502   -92.4874
0.8407    155.7895
0.8257    141.8158
1.0035     1.9178
0.9034    169.9910
0.8829   -153.1700
0.7636    149.3314
RMSE = 1x2
0.1304    141.1155
idfault =
7
Ifpolar = 1x2
1.4431    89.8954
Vpolar = 9x2
0.1092    174.4762
0.1694    105.7093
0.0955    123.1476
0.1265   -165.8622
0.1439   -156.0517
0.0551    146.4226
0.0000   -90.0000
0.0717    121.6723
0.1555   -155.8001
Vpolar_diff = 9x2

```

```

0.8909 -174.4822
0.8308 -96.0455
0.9045 -118.3823
0.8606 163.4522
0.8317 152.0309
0.9483 -144.5049
0.9858 90.6152
0.9246 -117.8805
0.8023 151.4464
RMSE = 1x2
0.1149 140.3415
idfault =
8
Ifpolar = 1x2
1.4610 93.0408
Vpolar = 9x2
0.1227 -154.7548
0.1023 94.5962
0.0985 165.3541
0.1562 -143.1117
0.1909 -141.1043
0.0923 -164.5400
0.0769 -137.8407
0.0000 0
0.1815 -135.9673
Vpolar_diff = 9x2
0.8774 154.7488
0.8978 -84.9325
0.9016 -160.5888
0.8309 140.7017
0.7847 137.0835
0.9112 166.4578
0.9089 138.4559
0.9963 3.7918
0.7763 131.6137
RMSE = 1x2
0.1262 135.4792
idfault =
9
Ifpolar = 1x2
1.4077 84.8158
Vpolar = 9x2
0.0840 94.7024
0.2725 101.9756
0.2056 113.1638
0.0472 116.1451
0.0793 159.9429
0.1582 118.1234
0.1389 124.8042
0.1715 106.3706
0 0
Vpolar_diff = 9x2
0.9161 -94.7084
0.7276 -92.3119
0.7945 -108.3985
0.9399 -118.5551
0.8964 -163.9637
0.8453 -116.2056
0.8469 -124.1890
0.8248 -102.5788
0.9578 -4.3537
RMSE = 1x2
0.1512 111.5990

```

```
% We notice that Vf(id fault) is always 0, since this is a node to gnd
% fault
% The magnitudes of Vf are around 20% of the V we found in part 1, i.e much
% lower due to the fault – this is expected due to a short.
% We calculate the RMSE between the vectors, and we notice that magnitudes
% drop the most for nodes 1,2,3 – which are the slack node, as well as the
% 2 nodes with the highest phase angle,
% meaning they generate reactive power.
```

```
% Question 4
% Load parameters for IEEE9_A1
```

```
run('ieee9_A1.m');
```

```
id = [3 5]'
```

```
id = 2x1
      3
      5
```

```
[Eeq, Zeq] = genthevenin(Y, Iint, id)
```

```
Eeq = 2x1 complex
      0.9966 + 0.0831i
      0.9732 - 0.0684i
Zeq = 2x2 complex
      0.0096 - 0.6249i   -0.0037 - 0.7475i
      -0.0037 - 0.7475i   0.0111 - 0.6810i
```

```
id = [9 4]'
```

```
id = 2x1
      9
      4
```

```
[Eeq, Zeq] = genthevenin(Y, Iint, id)
```

```
Eeq = 2x1 complex
      0.9550 - 0.0727i
      0.9862 - 0.0415i
Zeq = 2x2 complex
      0.0099 - 0.6803i   0.0053 - 0.7178i
      0.0053 - 0.7178i   0.0103 - 0.6801i
```

```
%Thevenin equivalent circuit attached at the end for 9/4 node system.
```

```
% Question 5
% Load parameters for IEEE9_A1
run('ieee9_A1.m');
```

```

%5.a
% Simulate outage at line 8
% remove elements in id 8
id = 8;
nfrom(id) = [];
nto(id)    = [];
r(id)      = [];
x(id)      = [];
b_temp = j*b(id);
b(id)      = [];

%Calculate Y for the IEEE9_A1 system with line 8 removed
Y = admittance(nfrom, nto, r, x, b);
V = Y \ Iint;
Vpolar = [abs(V), rad2deg(angle(V))]

```

```

Vpolar = 9x2
    1.2450    -7.4947
    1.3746    16.8116
    1.3218     6.8189
    1.2374    -9.4798
    1.2465    -6.8905
    1.3231     4.6576
    1.3242     7.6509
    1.3566    12.5839
    1.2038   -14.8331

```

%Disconnecting line 8 (connection between node 8 and 9) resulted in larger %voltages and angles in the system. This makes sense since the network %would have less impedance.

```

%5.a using gen fault
%Calculate Y for the IEEE9_A1 system – reset the values
run('ieee9_A1.m');

```

```

function YF = negative_yf(r, x, b)
    % Full cancellation for a single line
    y = 1/(r + 1j*x);    % series admittance
    yb = 1j*(b/2);       % half shunt at each end
    YF = -[ y + yb,  -y;
           -y,      y + yb ];
end

```

```

Y = admittance(nfrom, nto, r, x, b);
%Setup the parameters
YN = Y;
% we use the previous id we set up in part 1. it will be 8 here since line
% 8. We create a YF matrix that 'is opposite' to the YN matrix for the line
% we are cancelling, and we don't inject any current from the Fault side.
YF = negative_yf(r(id), x(id), b(id));
IintN = Iint;
IintF = [0,0]';

```

```

idN = [8 9]';
idF = [1 2]';
[IT, VNF] = genfault(YN, YF, IintN, IintF, idN, idF);
% The tie line currents for Node 1 as seen from the healthy network
IT;
ITpolar = [abs(IT), rad2deg(angle(IT))]
```

```

ITpolar = 2x2
    3.7529    179.4113
    3.7741    -6.3768
```

```

% The V for Node 1 and then other nodes as seen from the healthy network
VNF;
VNFpolar = [abs(VNF), rad2deg(angle(VNF))];
%Reorder to original order to compare
VNFpolar = VNFpolar([3:9 1 2], :)
```

```

VNFpolar = 9x2
    1.2450    -7.4947
    1.3746    16.8116
    1.3218     6.8189
    1.2374    -9.4798
    1.2465    -6.8905
    1.3231     4.6576
    1.3242     7.6509
    1.3566    12.5839
    1.2038   -14.8331
```

```

% We notice that using gen fault and 'removing the line' give the same
% result. IT is (almost) equal and opposite, the shunt terms deviate them a
% little.
```

%5.b

```

%Calculate Y for the IEEE9_A1 system – reset the values
run('ieee9_A1.m');
```

```

Y = admittance(nfrom, nto, r, x, b);
```

```

%Setup the parameters
```

```

YN = Y;
```

```

YF = Y;
```

```

IintN = Iint;
```

```

IintF = Iint;
```

```

%make the connections and calculate IT and VNF
```

```

idN = [1]';
```

```

idF = [5]';
```

```

[IT, VNF] = genfault(YN, YF, IintN, IintF, idN, idF);
```

```

% The tie line currents for Node 1 as seen from the healthy network
```

```

IT;
```

```

ITpolar = [abs(IT), rad2deg(angle(IT))]
```

```

ITpolar = 1x2
```


0.0563 157.5645

```
% The V for Node 1 and then other nodes as seen from the healthy network
VNF;
VNFpolar = [abs(VNF), rad2deg(angle(VNF))]
```

```
VNFpolar = 9x2
    0.9878    -1.8985
    0.9778     7.5432
    0.9809     2.5375
    0.9752    -4.5362
    0.9638    -6.3143
    0.9862    -0.3529
    0.9694    -1.7310
    0.9779     1.5446
    0.9463    -6.6865
```

%5.c

```
%make the connections and calculate IT and VNF
idN = [3 5]';
idF = [7 4]';
[IT, VNF] = genfault(YN, YF, IintN, IintF, idN, idF);
% The tie line currents for Nodes 3,5 as seen from the healthy network
IT;
ITpolar = [abs(IT), rad2deg(angle(IT))]
```

```
ITpolar = 2x2
    0.2735    -4.3887
    0.2842   175.9323
```

```
% The V for Nodes 3,5 and then other nodes as seen from the healthy network
VNF;
VNFpolar = [abs(VNF), rad2deg(angle(VNF))]
```

```
VNFpolar = 9x2
    0.9918     2.4182
    0.9810    -3.3848
    1.0042     0.2179
    0.9965     8.9018
    0.9910    -2.1735
    0.9985     0.4780
    0.9830    -0.4697
    0.9941     3.0101
    0.9605    -4.4756
```

%5.d

```
% Load parameters for IEEE24_A1
run('ieee24_A1.m');
```

```
%Calculate Y for the IEEE24_A1 system
Y = admittance(nfrom, nto, r, x, b);
```

```
%Setup the parameters
```

```
YN = Y;
```

```
YF = Y;
```

```
IintN = Iint;
```

```
IintF = Iint;
```

```
%make the connections and calculate IT and VNF
```

```
idN = [7 13 23]';
```

```
idF = [3 15 17]';
```

```
[IT, VNF] = genfault(YN, YF, IintN, IintF, idN, idF);
```

```
% The tie line currents for Nodes 7,13,23 as seen from the healthy network  
IT;
```

```
ITpolar = [abs(IT), rad2deg(angle(IT))]
```

```
ITpolar = 3×2
```

```
0.6285 5.0002
```

```
2.0075 -176.1139
```

```
1.8032 4.8616
```

```
% The V for Nodes 7,13,23 and then other nodes as seen from the healthy  
network
```

```
VNF;
```

```
VNFpolar = [abs(VNF), rad2deg(angle(VNF))]
```

```
VNFpolar = 24×2
```

```
0.9957 -8.7532
```

```
1.0131 6.6780
```

```
1.0409 12.4247
```

```
1.0117 -4.5223
```

```
1.0115 -4.8092
```

```
0.9522 -1.5813
```

```
0.9650 -6.4771
```

```
1.0017 -6.5348
```

```
0.9788 -13.4075
```

```
0.9651 -10.2640
```

```
0.9660 -3.6608
```

```
1.0224 -5.4746
```

```
0.9842 2.1057
```

```
0.9999 2.9917
```

```
0.9672 4.8457
```

```
⋮
```